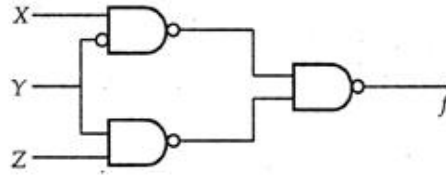


DIGITAL LOGIC

SOLUTIONS

1. Consider the following circuit:



Which one of the following is TRUE?

- (a) f is independent of X
- (b) f is independent of Y
- (c) f is independent of Z
- (d) None of X, Y, Z is redundant

Solution: Option (a)

2. Consider numbers represented in 4-bit gray code. Let $h_3h_2h_1h_0$ be the gray code representation of a number n and let $g_3g_2g_1g_0$ be the gray code of $(n + 1)$ (modulo 16) value of the number. Which one of the following functions is correct?

- (a) $g_0(h_3, h_2, h_1, h_0) = \Sigma(1, 2, 3, 6, 10, 13, 14, 15)$
- (b) $g_1(h_3, h_2, h_1, h_0) = \Sigma(4, 9, 10, 11, 12, 13, 14, 15)$
- (c) $g_2(h_3, h_2, h_1, h_0) = \Sigma(2, 4, 5, 6, 7, 12, 13, 15)$
- (d) $g_3(h_3, h_2, h_1, h_0) = \Sigma(0, 1, 6, 7, 10, 11, 12, 13)$

Solution: Option (c)

3. We consider the addition of two 2's complement numbers $b_{n-1}b_{n-2}\dots b_0$ and $a_{n-1}a_{n-2}\dots a_0$. A binary adder for adding unsigned binary numbers is used to add the two numbers. The sum is denoted by $c_{n-1}c_{n-2}\dots c_0$ and the carry-out by c_{out} . Which one of the following options correctly identifies the overflow condition?

- (a) $c_{out}(\overline{a_{n-1}} \oplus \overline{b_{n-1}})$
- (b) $a_{n-1}b_{n-1}\overline{c_{n-1}} + \overline{a_{n-1}}\overline{b_{n-1}}c_{n-1}$
- (c) $\overline{c_{out}} \oplus c_{n-1}$
- (d) $\overline{a_{n-1}} \oplus \overline{b_{n-1}} \oplus c_{n-1}$

Solution: Option (b)

4. Consider a Boolean function $f(w, x, y, z)$. suppose that exactly one of its inputs is allowed to change at a time. If the function happens to be true for two input vectors $i_1 = (w_1, x_1, y_1, z_1)$ and $i_2 = (w_2, x_2, y_2, z_2)$ we would like the function to remain true as the input changes from i_1 to i_2 (i_1 and i_2 differ in exactly one bit position), without becoming false momentarily.

$$\text{Let } f(w, x, y, z) = \sum(5, 7, 11, 12, 13, 15).$$

Which of the following cube covers of f will ensure that the required property is satisfied?

(a) $w'xz, wxy', xy'z, xyz, wyz$


(b) $wxy, w'xz, wyz$

(c) $wx(yz)', xz, wx'yz$

(d) $wzy, wyz, wxz, w'xz, xy'z, xyz$

Solution: Option (a)

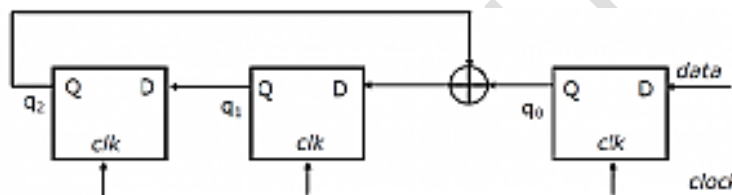5. Consider the circuit in the diagram. The \oplus operator represents Ex-OR. The D flipflops are initialized to zeroes (cleared).



The following data: 100110000 is supplied to the “data” terminal in nine clock cycles. After that the values of $q_2q_1q_0$ are:

(a) 000

(b) 001

(c) 010

(d) 101

Solution: Option (c)

6. Given two three bit numbers $a_2a_1a_0$ and $b_2b_1b_0$ and c , the carry in, the function that represents the carry generate function when these two numbers are added is:

(a) $a_2b_2 + a_2a_1b_1 + a_2a_1a_0b_0 + a_2a_0b_1b_0 + a_1b_2b_1 + a_2a_0b_2b_0 + a_0b_2b_1b_0$


(b) $a_2b_2 + a_2b_1b_0 + a_2a_1b_1b_0 + a_1a_0b_2b_1 + a_1a_0b_2 + a_1a_0b_2b_0 + a_2a_0b_2b_0$

(c) $a_2 + b_2 + (a_2 \oplus b_2)(a_1 + b_1 + (a_1 \oplus b_1)(a_0 + b_0))$

(d) $a_2b_2 + \overline{a_2}a_1b_1 + \overline{a_2}\overline{a_1}a_0b_0 + \overline{a_2}a_0\overline{b_1}b_0 + a_1\overline{b_2}b_1 + \overline{a_1}a_0\overline{b_2}b_0 + a_0\overline{b_2}b_1b_0$

Solution: Option (a)

7.

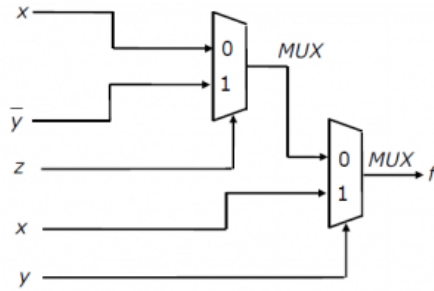

Consider the circuit above. Which one of the following options correctly represents $f(x, y, z)$?

- (a) $xz' + xy + y'z$ (b) $xz' + xy + (yz)'$
(c) $xz + xy + (yz)'$ (d) $xz + xy' + y'z$

Solution: Option (a)

8. Let X denote the Exclusive OR (XOR) operation. Let '1' and '0' denote the binary constants. Consider the following Boolean expression for F over two variables P and Q:


$$F(P, Q) = ((1 \times P) \times (P \times Q)) \times ((P \times Q) \times (Q \times 0))$$

The equivalent expression for F is

- (a) $P + Q$ (b) $(P + Q)'$
(c) $P \times Q$ (d) $(P \times Q)'$

Solution: Option (d)

9.

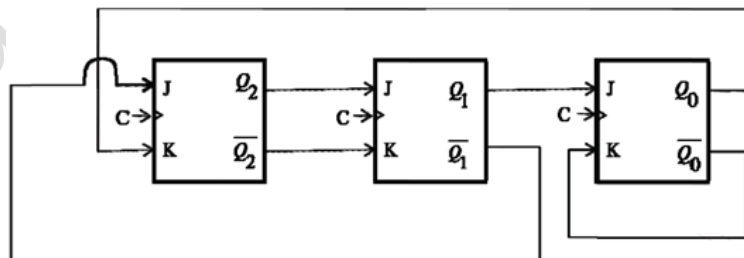

The above sequential circuit is built using JK flip-flops is initialized with $Q_2Q_1Q_0 = 000$. The state sequence for this circuit for the next 3 clock cycle is

- (a) 001, 010, 011
(c) 100, 110, 111

- (b) 111, 110, 101
(d) 100, 011, 001

Solution: Option (c)

10. Consider the following combinational function block involving four Boolean variables x, y, a, b where x, a, b are inputs and y is the output.

$f(x, y, a, b)$
{
 if (x is 1) $y = a$;
 else $y = b$;
}

Which one of the following digital logic blocks is the most suitable for implementing this function?

- (a) Full adder
(c) Multiplexor
(b) Priority encoder
(d) Flip-flop

Solution: Option (c)

11. Consider the following minterm expression for F:

$$F(P, Q, R, S) = \sum 0, 2, 5, 7, 8, 10, 13, 15$$

The minterms 2, 7, 8 and 13 are 'do not care' terms. The minimal sum-of-products form for F is

- (a) $Q\bar{S} + \bar{Q}S$
(c) $\bar{Q}\bar{R}\bar{S} + \bar{Q}R\bar{S} + Q\bar{R}S + QRS$
(b) $\bar{Q}\bar{S} + QS$
(d) $\bar{P}\bar{Q}\bar{S} + \bar{P}QS + PQS + P\bar{Q}\bar{S}$

Solution: Option (b)

12. Consider the equation $(123)_5 = (x8)_y$ with x and y as unknown. The number of possible solutions is _____.

- (a) 1
(c) 3
(b) 2
(d) 4


Solution: Option (c)

13. Let $k = 2^n$. A circuit is built by giving the output of an n -bit binary counter as input to an n -to- 2^n bit decoder. This circuit is equivalent to a

- (a) k -bit binary up counter.
- (b) k -bit binary down counter.
- (c) k -bit ring counter.
- (d) k -bit Johnson counter.

Solution: Option (c)

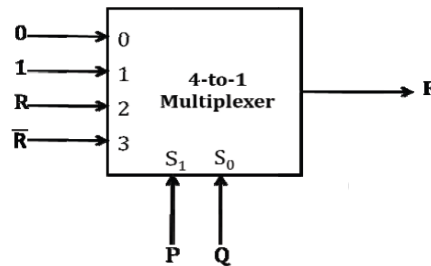14. Consider a 4-to-1 multiplexer with two select lines S_1 and S_0 , given below



The minimal sum-of-products form of the Boolean expression for the output F of the multiplexer is

- (a) $P'Q + QR' + PQ'R$
- (b) $P'Q + P'QR' + PQR' + PQ'R$
- (c) $P'QR + P'QR' + QR' + PQ'R$
- (d) PQR'

Solution: Option (a)

15. Consider the following Boolean expression for F :

$$F(P, Q, R, S) = PQ + \bar{P}QR + \bar{P}Q\bar{R}S$$


The minimal sum-of-products form of F is

- (a) $PQ + QR + QS$
- (b) $P + Q + R + S$
- (c) $\bar{P} + \bar{Q} + \bar{R} + \bar{S}$
- (d) $\bar{P}R + \bar{P}\bar{R}S + P$


Solution: Option (a)

16. You are given a free running clock with a duty cycle of 50% and a digital waveform f which changes only at the negative edge of the clock. Which one of the following circuits (using clocked D flip-flops) will delay the phase of f by 180° ?


(a)

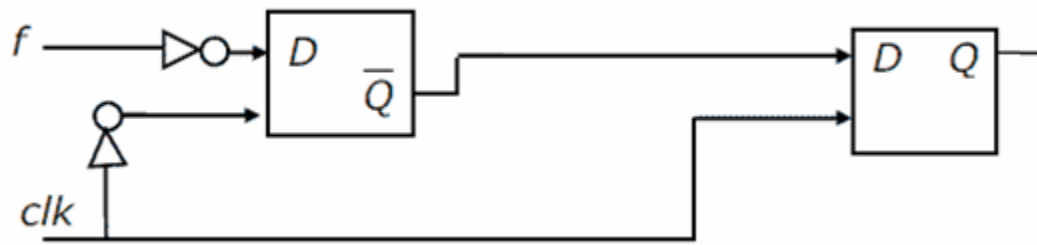


(b)

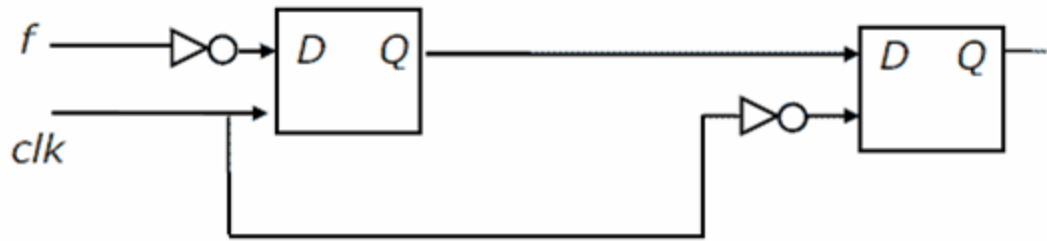

(c)

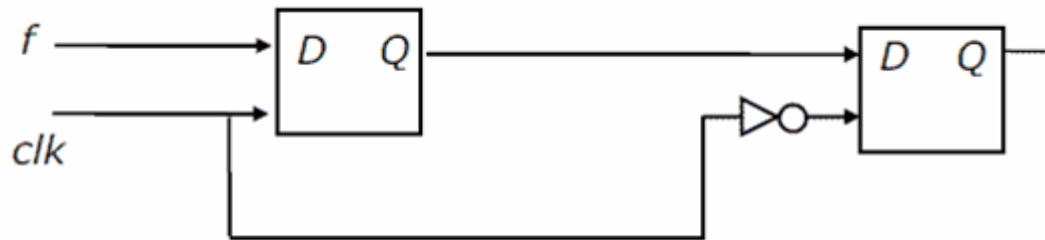

(d)

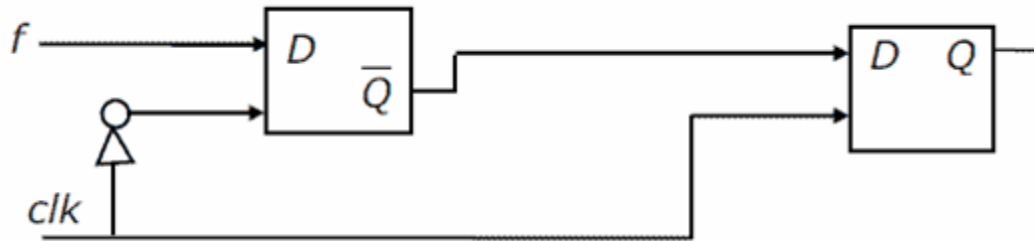

Solution: Option (c)

17. The control signal functions of a 4-bit binary counter are given below (where X is “don’t care”)

The counter is connected as follows:

Solution: Option (b)

19. Suppose only one multiplexer and one inverter are allowed to be used to implement any Boolean function of n variables. What is the minimum size of the multiplexer needed?

- (a) 2^n line to 1 line
- (b) 2^{n+1} line to 1 line
- (c) 2^{n-1} line to 1 line
- (d) 2^{n-2} line to 1 line

Solution: Option (c)

20. Define the connective $*$ for the Boolean variables X and Y as:

$$X * Y = XY + X'Y'. \text{ Let } Z = X * Y.$$

Consider the following expressions P , Q and R :

$$P: X = Y * Z$$

$$Q: Y = X * Z$$

$$R: X * Y * Z = 1$$

Which of the following is TRUE?

- (a) Only P and Q are valid.
- (b) Only Q and R are valid.
- (c) Only P and R are valid.
- (d) All P , Q , R are valid.

Solution: Option (d)