

DIGITAL LOGIC

SOLUTIONS

1. In the following truth table, $V = 1$ if and only if the input is valid.

Inputs				Outputs		
D_0	D_1	D_2	D_3	X_0	X_1	V
0	0	0	0	x	x	0
1	0	0	0	0	0	1
x	1	0	0	0	1	1
x	x	1	0	1	0	1
x	x	x	1	1	1	1

What function does the truth table represent?

- (a) Priority encoder
- (c) Multiplexer

- (b) Decoder
- (d) Demultiplexer

Solution: Option (a)

Explanation:

Since there are more than one outputs and number of outputs are less than inputs, it is a Priority encoder.

2. Which one of the following expressions does NOT represent exclusive NOR of x and y ?

- (a) $xy + x'y'$
- (c) $x' \wedge y$ where \wedge is XOR

- (b) $x \wedge y'$ where \wedge is XOR
- (d) $x' \wedge y'$ where \wedge is XOR

Solution: Option (d)

Explanation:

It is a simple De Morgan's laws question.

3. The truth table

X	Y	f(X, Y)
0	0	0
0	1	0
1	0	1
1	1	1

represents the Boolean function:

(a) X

(b) $X + Y$

(c) $X \text{ xor } Y$

(d) Y

Solution: Option (a)

Explanation:

The value of $f(X, Y)$ is same as X for all input pairs.

4. What is the minimal form of the Karnaugh map shown below? Assume that X denotes a don't care term.

		ab			
		cd	00	01	11
	00	1	X	X	1
	01	X			1
	11				
	10	1			X

(a) $b'd'$

(b) $b'd' + b'c'$

(c) $b'd' + a'b'c'd'$

(d) $b'd' + b'c' + c'd'$


Solution: Option (b)

Explanation:

	ab			
	00	01	11	10
cd				
00	1	X	X	1
01	X			1
11				
10	1			X

5. Which one of the following circuits is NOT equivalent to a 2-input XNOR (exclusive NOR) gate?


(a)

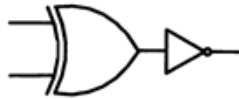


(b)



(c)

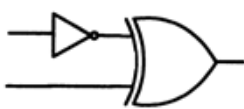

(d)

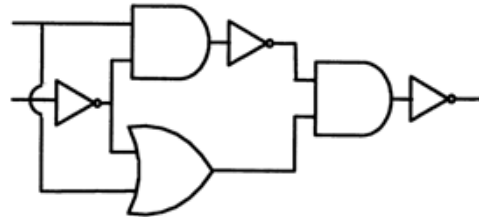

Solution: Option (d)

Explanation:

All options except D produce XOR.

6. The simplified SOP (Sum Of Product) form of the boolean expression $(P + Q' + R') \cdot (P + Q' + R) \cdot (P + Q + R')$ is

(a) $(P' \cdot Q + R')$


(b) $(P + Q' \cdot R')$

(c) $(P' \cdot Q + R)$

(d) $(P \cdot Q + R)$

Solution: Option (b)

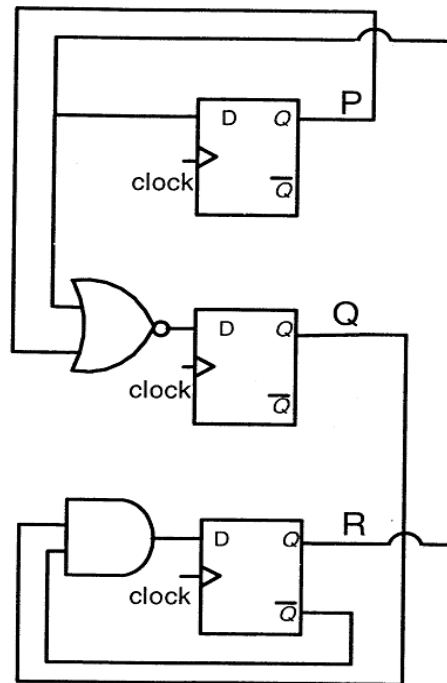7. Consider the following circuit involving three D-type flip-flops used in a certain type of counter configuration.



If at some instance prior to the occurrence of the clock edge, P, Q and R have a value 0, 1 and 0 respectively, what shall be the value of PQR after the clock edge?

- | | |
|---------|---------|
| (a) 000 | (b) 001 |
| (c) 010 | (d) 011 |

Solution: Option (d)

Explanation:

$$P' = R$$

$$Q' = (P + R)'$$

$$R' = QR'$$

Given that $(P, Q, R) = (0, 1, 0)$, next state $P', Q', R' = 0, 1, 1$

8. Consider the data given in previous question. If all the flip-flops were reset to 0 at power on, what is the total number of distinct outputs (states) represented by PQR generated by the counter?

- | | |
|-------|-------|
| (a) 3 | (b) 4 |
|-------|-------|

(c) 5

(d) 6

Solution: Option (b)

Explanation:

There are four distinct states, $000 \rightarrow 010 \rightarrow 011 \rightarrow 100 (\rightarrow 000)$

9. The minterm expansion of $f(P, Q, R) = PQ + QR' + PR'$ is

(a) $m_2 + m_4 + m_6 + m_7$


(b) $m_0 + m_1 + m_3 + m_5$

(c) $m_0 + m_1 + m_6 + m_7$

(d) $m_2 + m_3 + m_4 + m_5$

Solution: Option (a)

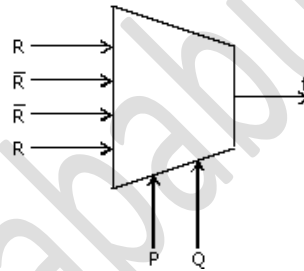10. The Boolean expression for the output 'f' of the multiplexer shown below is



(a) $(P(XOR) Q(XOR) R)'$


(b) $P(XOR) Q(XOR) R$

(c) $(P+Q+R)'$

(d) $P+Q+R$

Solution: Option (b)

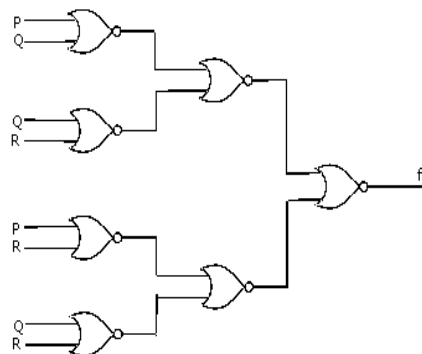11. What is the Boolean expression for the output f of the combinational logic circuit of NOR gates given below?




- (a) $(Q+R)'$
 (c) $(P+R)$

- (b) $(P+Q)'$
 (d) $(P+Q+R)'$

Solution: Option (a)

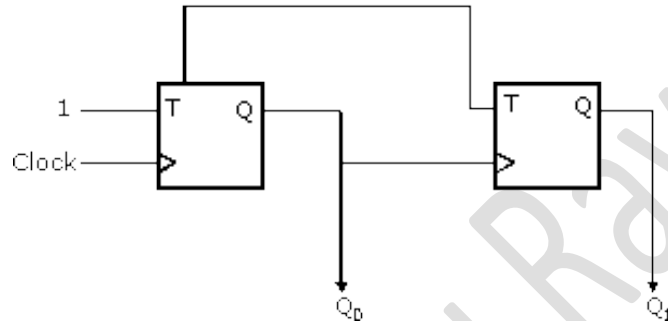12. In the sequential circuit shown below, if the initial value of the output Q_1Q_0 is 00, what are the next four values of Q_1Q_0 ?



- (a) 11, 10, 01, 00
 (c) 10, 00, 01, 11

- (b) 10, 11, 01, 00
 (d) 11, 10, 00, 01

Solution: Option (d)

13. In the Karnaugh map shown below, X denotes a don't care term. What is the minimal form of the function represented by the Karnaugh map?

		ab			
		00	01	11	10
cd	00	1	1		1
	01	X			
	11	X			
	10	1	1		X

- (a) $\bar{b} \cdot \bar{d} + \bar{a} \cdot \bar{d}$
 (c) $b'd' + a'bd'$

- (b) $a'b' + b'd' + a'bd'$
 (d) $a'b' + b'd' + a'd'$

Solution: Option (a)

14. What is the minimum number of gates required to implement the Boolean function $(AB+C)$ if we have to use only 2-input NOR gates?

- (a) 2 (b) 3
(c) 4 (d) 5

Solution: Option (b)

Explanation:

$$AB + C = (A+C) (B+C) = ((A+C)' + (B+C)')'$$


So, '3' 2-input NOR gates are required.

15. Let r denote number system radix. The only value(s) of r that satisfy the equation $\sqrt{121_r} = 11_r$ is/are

- (a) decimal 10 (b) decimal 11
(c) decimal 10 and 11 (d) any value > 2

Solution: Option (d)

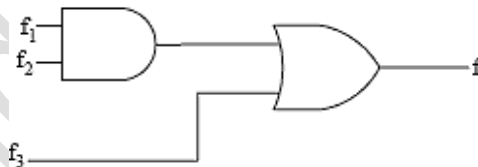16. Given f_1 , f_3 and f in canonical sum of products form (in decimal) for the circuit



$$f_1 = \Sigma m(4, 5, 6, 7, 8)$$

$$f_3 = \Sigma m(1, 6, 15)$$

$$f = \Sigma m(1, 6, 8, 15)$$

then f_2 is

- (a) $\Sigma m(4, 6)$ (b) $\Sigma m(4, 8)$
(c) $\Sigma m(6, 8)$ (d) $\Sigma m(4, 6, 8)$

Solution: Option (c)

17. If P , Q , R are Boolean variables, then $(P + Q')(PQ' + PR)(P'R' + Q')$ simplifies

(a) PQ'

(c) $PQ' + R$

(b) PR'

(d) $PR'' + Q$

Solution: Option (a)

18. How many 3-to-8 line decoders with an enable input are needed to construct a 6-to-64 line decoder without using any other logic gates?

(a) 7

(c) 9

(b) 8

(d) 10

Solution: Option (c)

19. Consider the following Boolean function of four variables:

$$f(w,x,y,z) = \sum(1,3,4,6,9,11,12,14)$$

The function is:

(a) independent of one variables.

(c) independent of three variables.

(b) independent of two variables.

(d) dependent on all the variables.

Solution: Option (b)

20. Let $f(w, x, y, z) = \sum(0, 4, 5, 7, 8, 9, 13, 15)$. Which of the following expressions are NOT equivalent to f ?

(a) $x'y'z' + w'xy' + wy'z + xz$

(c) $w'y'z' + wx'y' + xyz + xy'z$

(b) $w'y'z' + wx'y' + xz$

(d) $x'y'z' + wx'y' + w'y$

Solution: Option (d)